



# **250 W PFC LD7592GS & LD7932RG**

By : Jason Liao


Date : 2019/01/29

- 1. Specification**
- 2. Schematic**
- 3. PCB Layout**
- 4. Bill of Materials**
- 5. Transformer Design**
- 6. Efficiency & Power Factor**
- 7. Key Waveform**
- 8. Stress on Switching Parts**
- 9. Load Regulation**

# 1. Specification


Item	Min.	Typ.		Max.	Test Result
<b>Input Voltage ( V<sub>AC</sub> )</b>	90	115	230	264	—
<b>Input Frequency ( Hz )</b>	47	60	50	63	—
<b>Output Voltage &amp; Current ( V / A )</b>	390V/0.62A		5V/2A		—
<b>Efficiency</b>	>90%				Pass
<b>Power Factor</b>	>0.9				Pass
<b>Stress</b>	<90%				Pass
<b>Regulation</b>	385V~405V				Pass

# 2. Schematic

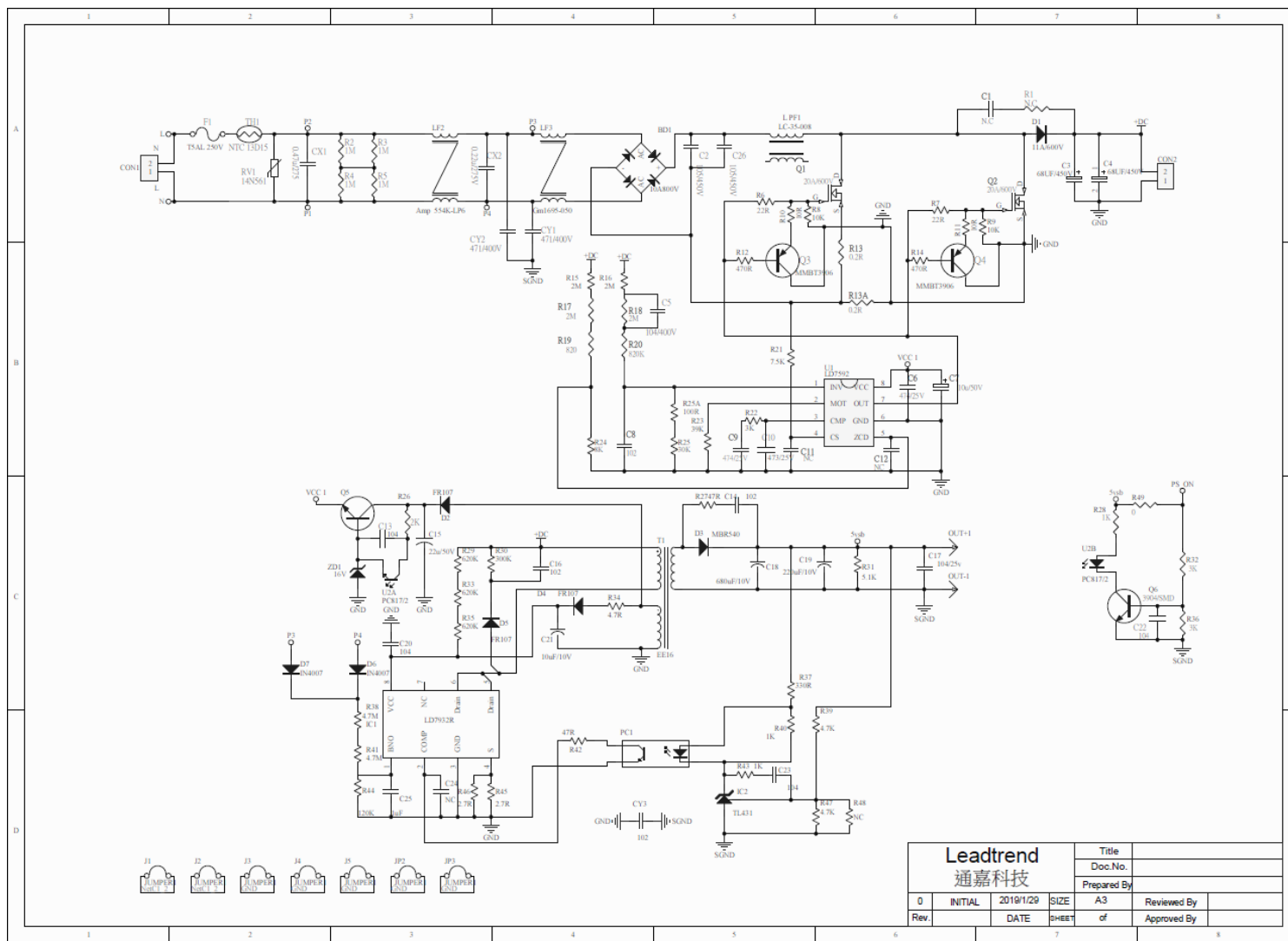

<b>Leadtrend</b>				Title	
通嘉科技				Doc.No	
				Prepared By	
0	INITIAL	2019/1/29	SIZE	A3	Reviewed By
Rev.	DATE	SHEET	of	Approved By	

# 3. PCB Layout

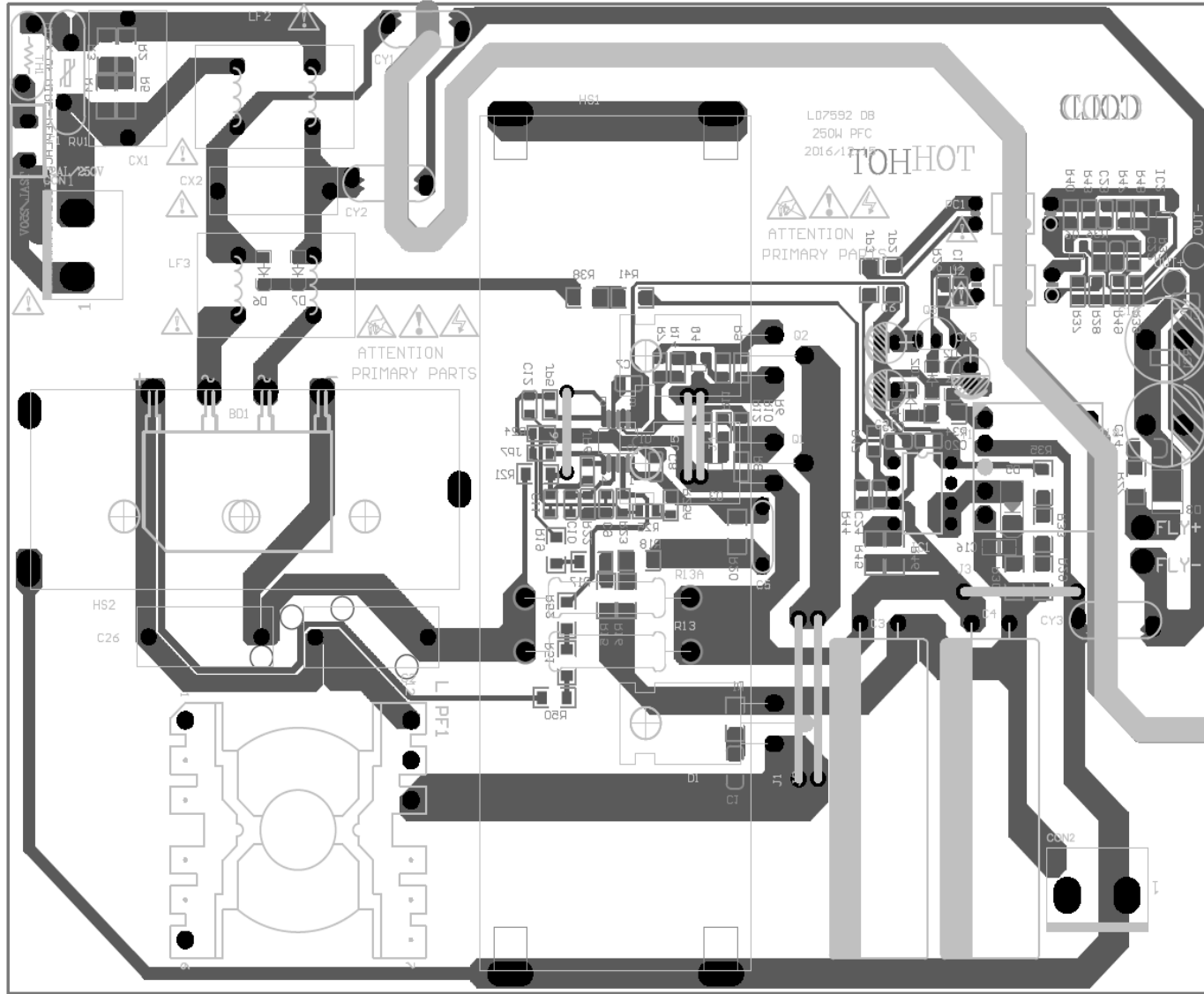

# 4. Bill of Materials

Location	Description	Q'ty
TH1	SCK208R0	1
R2,R3,R4,R5	SMD RES 1206 1M 5%	4
R6,R7	SMD RES 0805 22R 5%	2
R8,R9	SMD RES 0805 10K 5%	2
R10,R11	SMD RES 0805 10R 5%	2
R12,R14	SMD RES 0805 470R 5%	2
R13,R13A	0.2Ω / DIP-2W MOF 5%	2
R15,R16,R17,R18	SMD RES 1206 2M 5%	4
R19,R20	SMD RES 1206 820K 5%	2
R21	SMD RES 1206 7.5K 5%	1
R22,R32,R36	SMD RES 0805 3K 5%	3
R23	SMD RES 0805 39K 5%	1
R24,R25	SMD RES 0805 30K 5%	2
R25A	SMD RES 0805 100R 5%	1
R26	SMD RES 0805 2K 5%	1
R27	SMD RES 1206 47R 5%	2
R28,R40,R43	SMD RES 0805 1K 5%	3
R29,R33,R35	SMD RES 1206 620K 5%	3
R30	SMD RES 1206 300K 5%	1
R31	SMD RES 0805 5.1K 5%	1
R34	SMD RES 1206 4.7R 5%	1
R37	SMD RES 0805 330R 5%	1
R38,R41	SMD RES 1206 4.7MF 1%	2
R39,R47	SMD RES 0805 4.7K 5%	2
R42	SMD RES 0805 4.7R 5%	1
R44	SMD RES 0805 120KF 1%	1
R44,R45	SMD RES 1206 2.7RF 1%	2
R49	SMD RES 0805 0R 5%	1
JP2,JP3,JP5,JP6	SMD RES 1206 0R 5%	4
CY1,CY2	470 pF ( 471 ) / 250V	2
CY3	Y1 CAP CD 102 250V P:10mm 20%, CD70ZU2GA102MYPKA,帶裝	1


Location	Description	Q'ty
C6,C21	E CAP 10uF 50V SY 20% 5*11 P:2.0mm	2
C8	SMD CC 0805 471 50V X7R 10%	1
C9	SMD CC 0805 684 50V X7R 10%	1
C10	SMD CC 0805 473 50V X7R 10%	1
C13,C17,C20,C22,C23	SMD CC 0805 104 50V X7R 10%	5
C14	SMD CC 1206 102 1000V X7R 10%	1
C15	E CAP 22uF 50V SY 20% 5*11 P:2.0mm	1
C5,C16	DIP CC 222 1KV Y5P ±10%	2
C18,C19	E CAP 470uF 25V SC 10*12 P:5.0mm	2
C25	SMD CC 0805 105 50V Y5V	1
CX1	DIP X2 CAP HQX 0.47uF(474) ±10% 275V P:15mm(17*16*10.3mm)	1
CX2	DIP X2 CAP HQX 0.22UF(224) ±10% 275Vac 6*14*17mm P:15mm(腳長更正為3.5mm)	1
BD1	HY GBJ1008	1
D2,D4,D5,D6,D7	FRS1ME	5
D3	威倫 MBR1045ULPS	1
IC1	LD7932R / DIP-8	1
IC2	SMD IC LA431OCRPA SOT-23-3L	1
Q1,Q2	AUK SJMN190R65F	2
Q3,Q4	MMBT3906	2
Q5	UTC 2N5551	1
Q6	MMBT3904	1
U1	LD7592 / SOP-8	1
PC1,U2	DIP IC EL817C (CTR 200-400)	2
RV1	14N561	1
T1	EE-16加寬 / AE 38 / 65:4:15 / 1800 uH	1
LF2,LF3	ESQ2418GRP2L-802-E10	2
PF1	EQ40 / 0.1*70*38T L= 230uh	1
F1	DIP FUSE 5A 250V 2010 Time Lag 8.5*8.5*4mm 方型塑膠外殼	1
ZD1	BZT52-C16	1

# 4. Bill of Materials

Location	Description	Q'ty
D1	TI STTH10LCD06FP	1
C3,C4	智寶 SQ 82uF/450V/12.5*40	2
PCB	160 x 124 x 2 mm / FR-4 / 2 oz	1
C2,C26	105/450V/朱肝電容/18*7.5*15mm	2
C7	SMD CC 0805 224 50V X7R 10%	1
J1,J2	JUMP / 20mm / 1 Φ	2
J3	JUMP / 15mm / 1 Φ	1
J4,J5	JUMP / 10mm / 1 Φ	2
HS1	散熱片 / 107*35*5mm /	1
HS2	散熱片 / 60*25*7mm /	1
CON1,CON2	Pitch = 3.96 mm ( 3 PIN Cut pin2 )	2
FOR HS1,HS2	Screw, M3x10L ,I頭,機械牙,鍍鋅,加耐落膠	4


# 5. Transformer Design

PF1

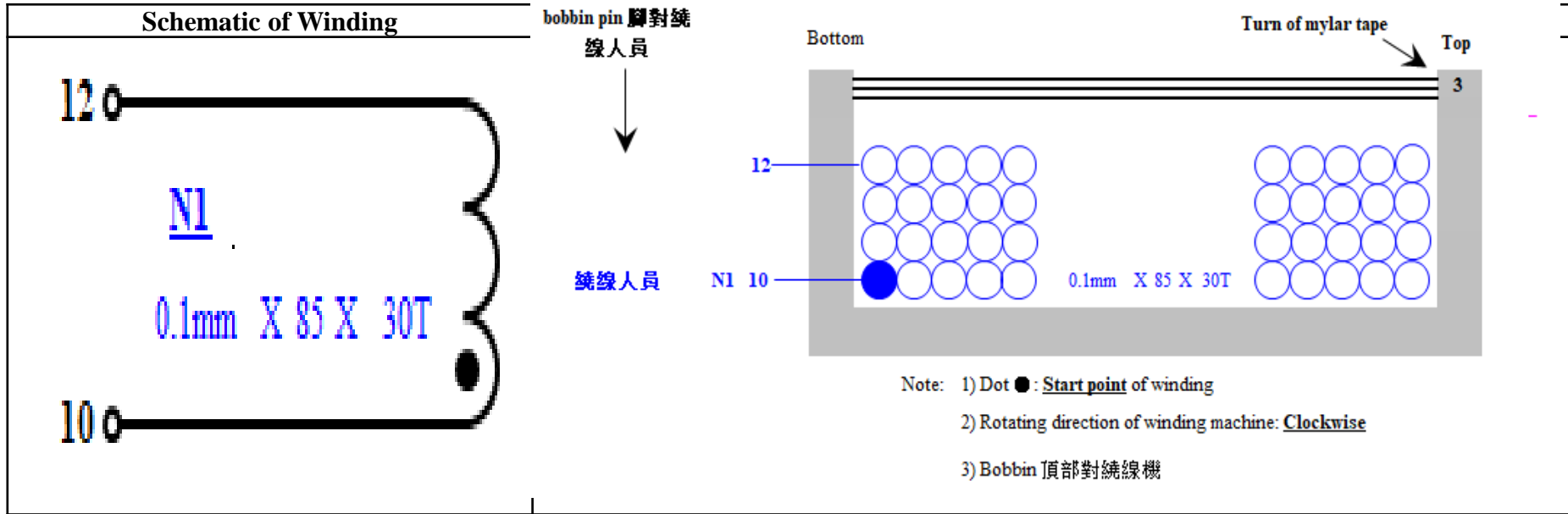

Winding No.	Pin No.		Winding Types	Number of Turns		Remarks	
	Start	Finis h		Winding	Tape		
N1	10	12	0.1 mm X 85	30	3	N1	Pin 朝人順繞


Bobbin Shape	Core Material	$A_e$ (mm <sup>2</sup> )	$L_p$ (μH)
PQ3225	PC44	149	170 ± 5 % @ 65 kHz / 1 V

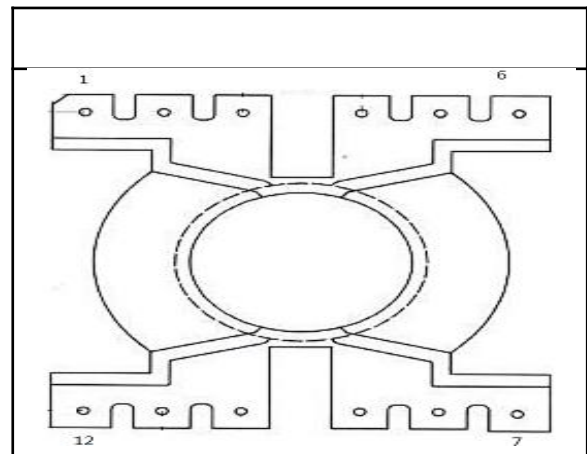




# 5. Transformer Design

T1

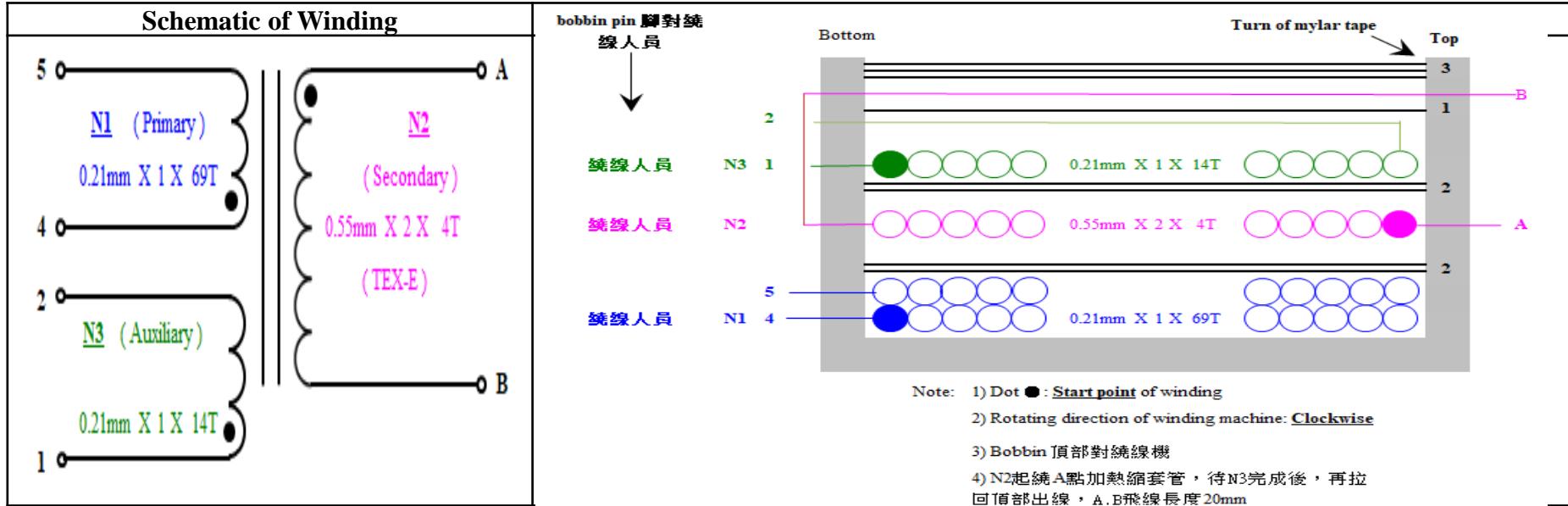

Winding No.	Pin No.		Winding Types	Number of Turns		Remarks	
	Start	Finish		Winding	Tape		
N1	4	5	0.21 mm X 1	69	2	$N_p$	Pin 朝人順繞
N2	A	B	0.55 mm X 2	4	2	$N_s$	Pin 朝人順繞
N3	1	2	0.21 mm X 1	14	1	$N_a$	Pin 朝人順繞(疏繞)

二次側線由頂部凹槽出線，起繞A點加熱縮套管

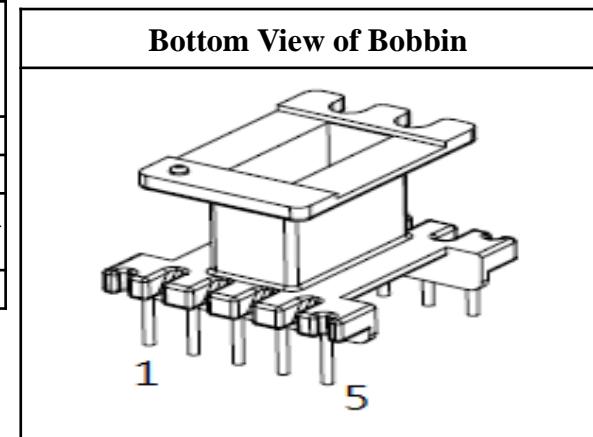


Bobbin Shape	Core Material	$A_e$ (mm <sup>2</sup> )	$L_p$ (μH)
EE-16W	PC44	38	1800 ± 5 % @ 65 kHz / 1 V

# 6. Efficiency & Power Factor


<b>Input Voltage</b>	90 V <sub>AC</sub> / 47 Hz 115 V <sub>AC</sub> / 60Hz 230 V <sub>AC</sub> / 50 Hz 264 V <sub>AC</sub> / 63 Hz
<b>Output Current</b>	Full Load
<b>Measured Point of Output Voltage</b>	End of PCB

<b>Voltage ( V )</b>	<b>Efficiency ( % )</b>	<b>Power Factor</b>
<b>90</b>	-	0.998
<b>115</b>	93.06%	0.996
<b>230</b>	97.45%	0.944
<b>264</b>	-	0.922


# 7. Key Waveform

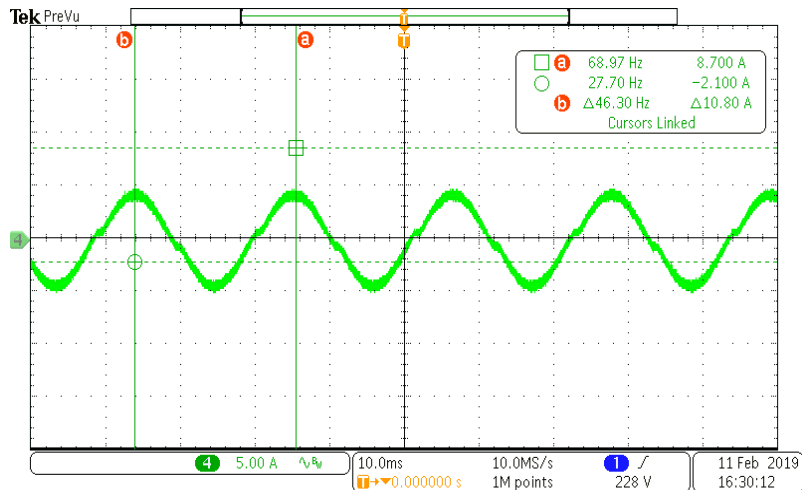


90Vac AC Current Waveform

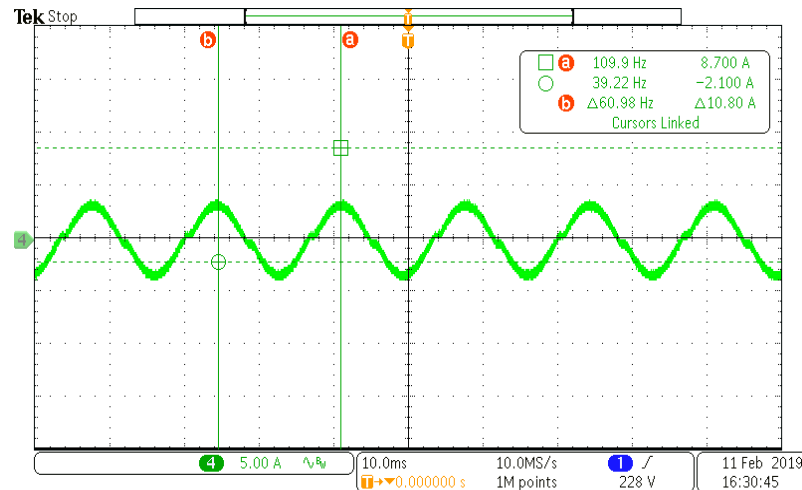

115Vac AC Current Waveform


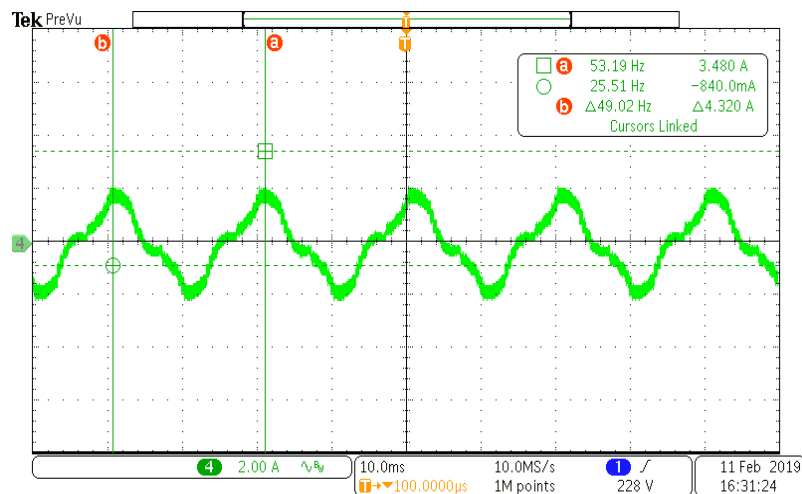


230Vac AC Current Waveform


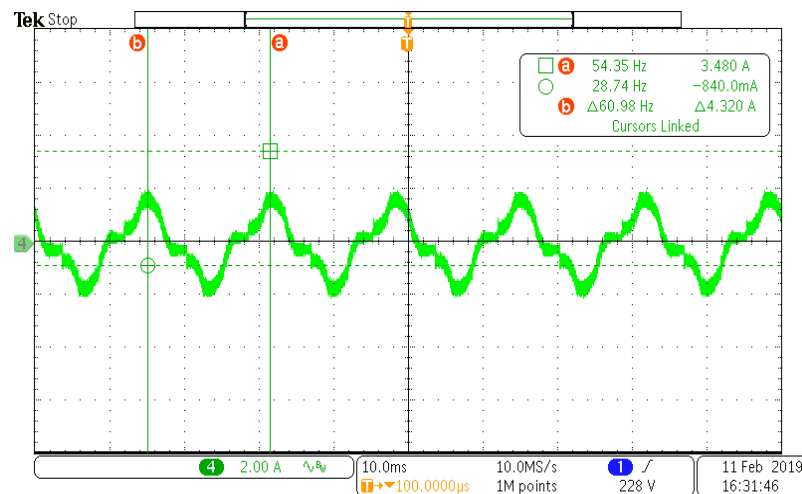


264Vac AC Current Waveform

# 7. Key Waveform

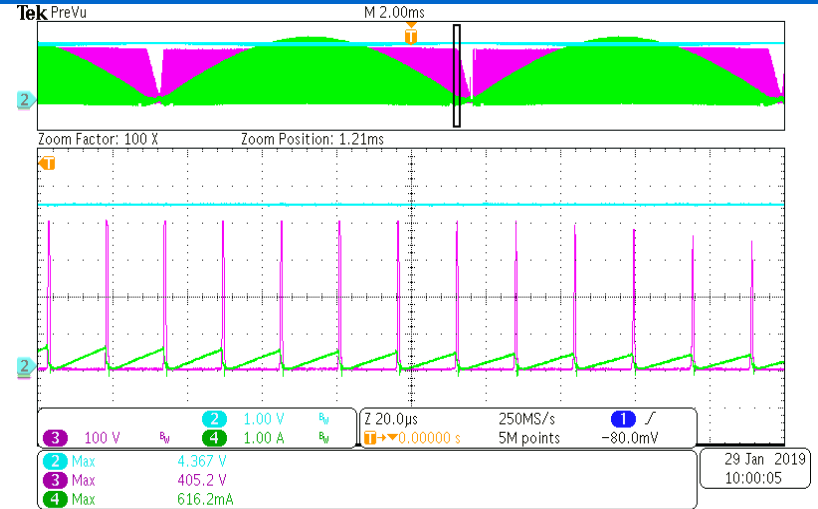
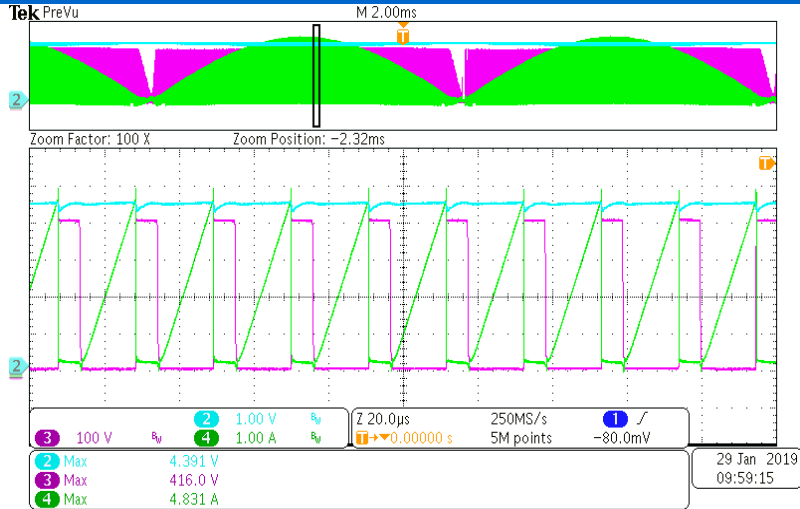


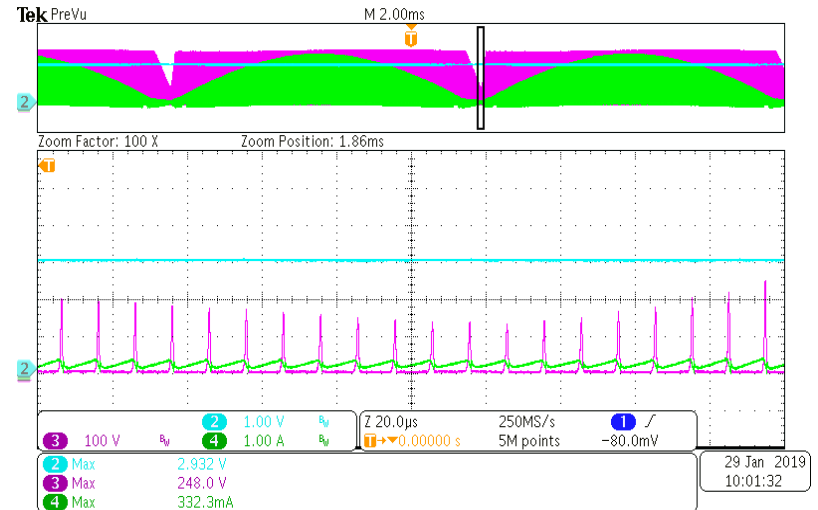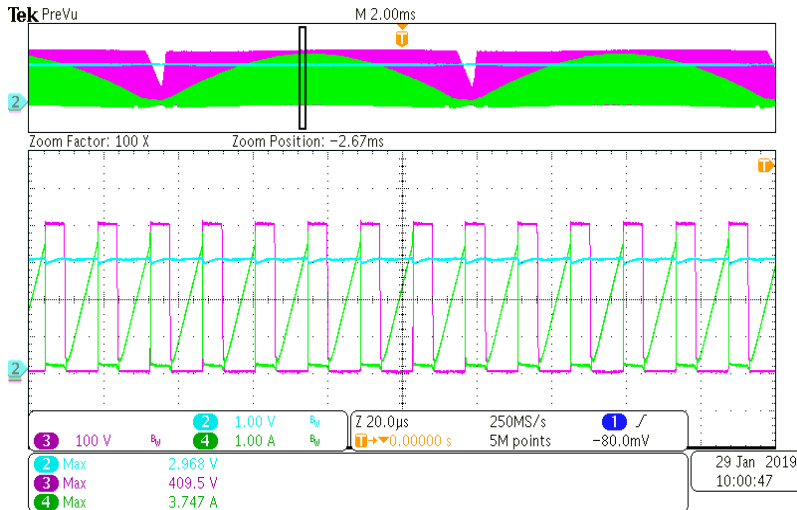90Vac 390V/0.62A , CH2 Comp . CH3  $V_{DS}$  . CH4  $I_{DS}$





115Vac 390V/0.62A , CH2 Comp . CH3  $V_{DS}$  . CH4  $I_{DS}$

# 7. Key Waveform

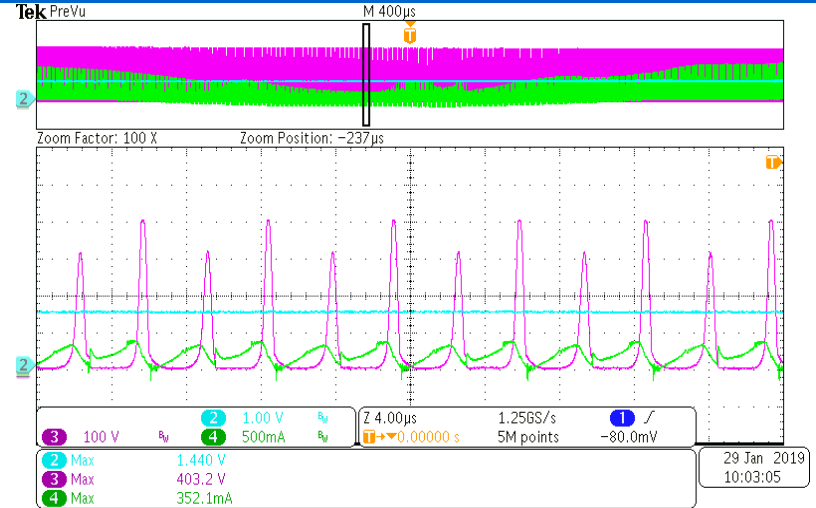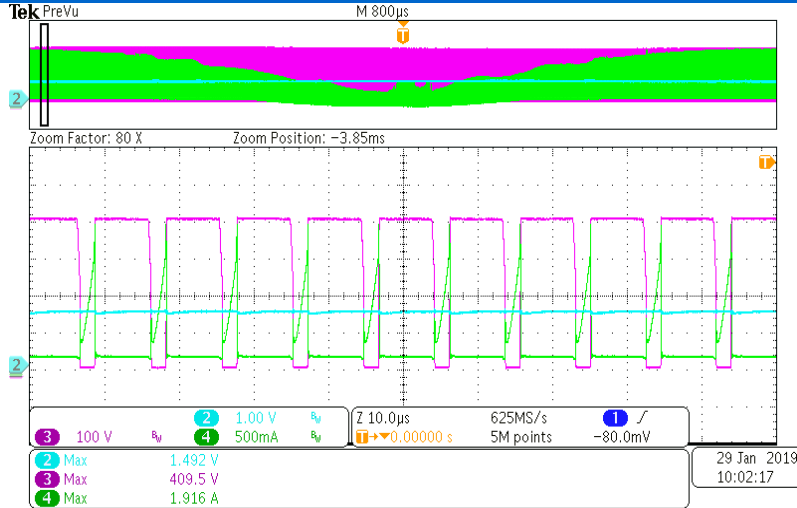


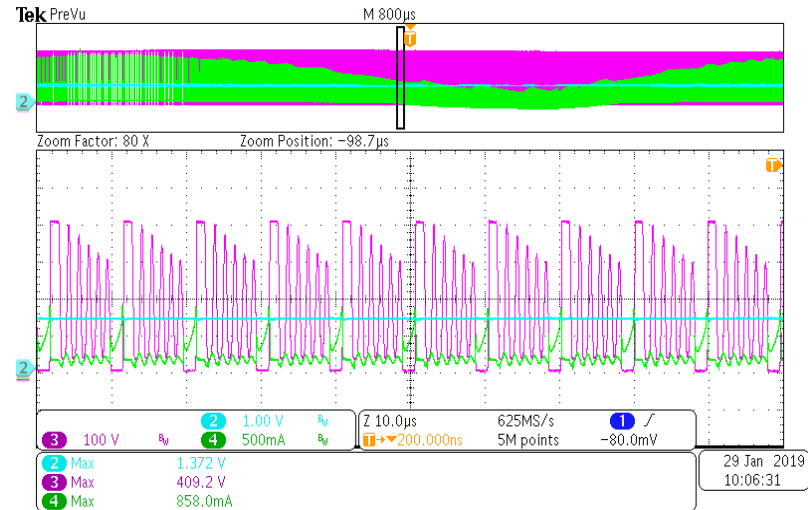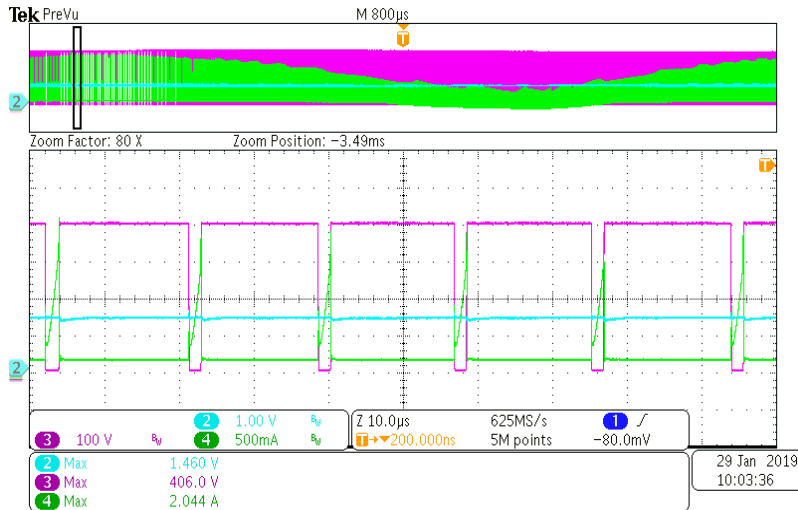230Vac 390V/0.62A , CH2 Comp . CH3  $V_{DS}$  . CH4  $I_{DS}$




264Vac 390V/0.62A , CH2 Comp . CH3  $V_{DS}$  . CH4  $I_{DS}$


# 7. Key Waveform

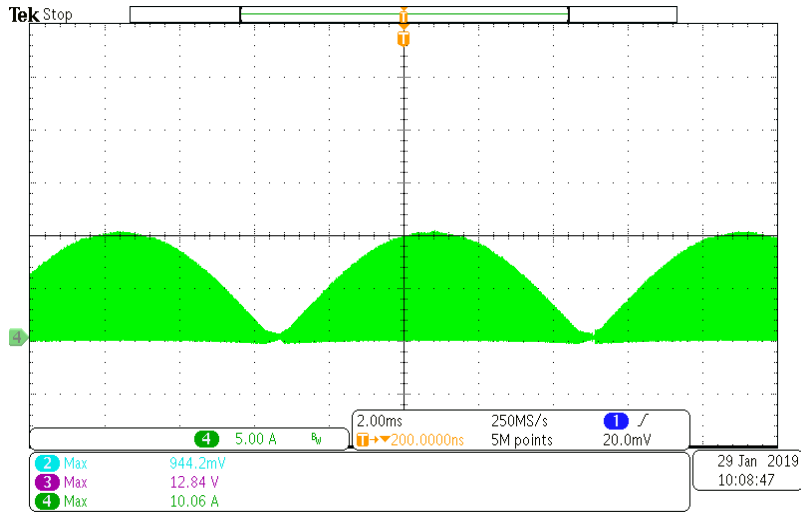


90Vac PFC Current Waveform

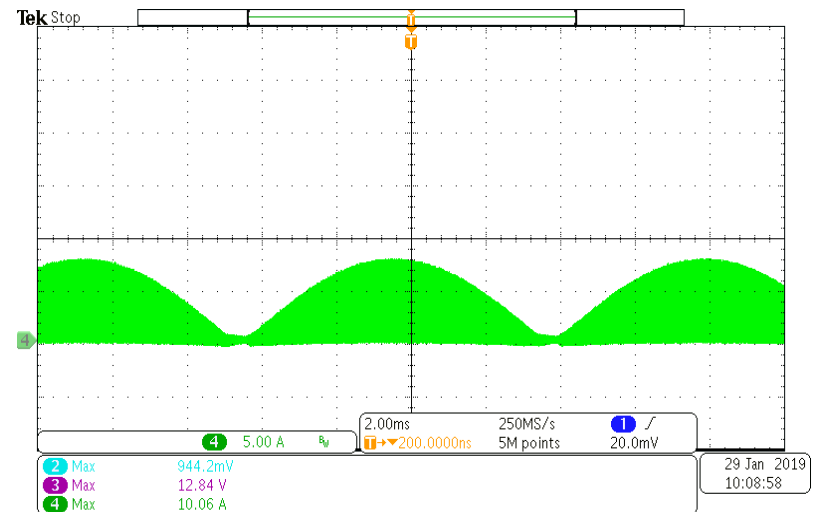

115Vac PFC Current Waveform

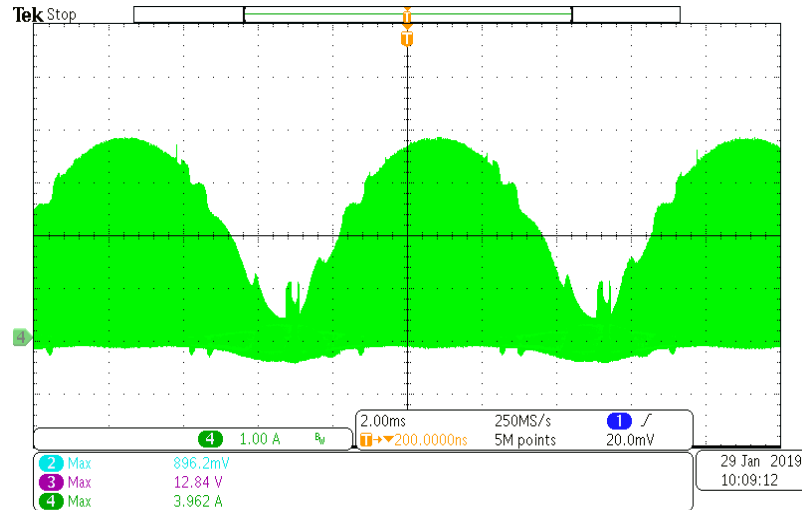

230Vac PFC Current Waveform

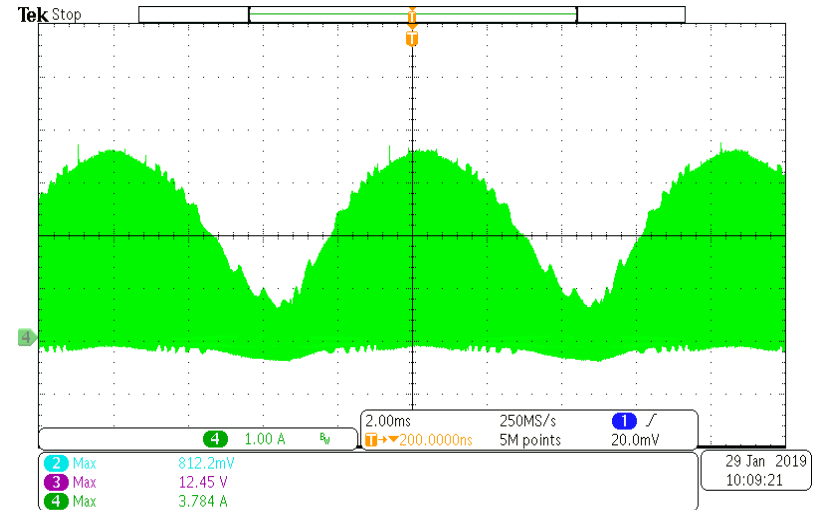

264Vac PFC Current Waveform

# 8. Stress on Switching Parts

<b>Input Voltage</b>	264 V <sub>AC</sub> / 63 Hz
<b>Output Current</b>	Full Load
<b>Requirement</b>	<90 %

NO.	Location	Voltage	Normal (264/60Hz)	
			Measurement	Derating
			V	%
1	Q1	600	446	74.3
2	D1	600	430	71.6

NO.	Location	Voltage	Turn on (264V/60Hz)	
			Measurement	Derating
			V	%
1	Q1	600	462	77.0
2	D1	600	438	73.0

# 9. Load Regulation

<b>Input Voltage</b>	90 V <sub>AC</sub> / 47 Hz	115 V <sub>AC</sub> / 60 Hz	230 V <sub>AC</sub> / 50 Hz	264 V <sub>AC</sub> / 63 Hz
<b>Output Current</b>	No Load & Full Load			
<b>Requirement</b>	385~405V			

( V / Hz )	( V )		Requirement ( V )
	No Load	Full Load	
90 / 47	400	399	385~405V
115 / 60	400	399	
230 / 50	400	399	
264 / 63	400	399	



# The Best Company for AC-DC Mid & High Power Application Total Solution



**THANK YOU**

